

Documentation
Hammer
Date: 24/06/2022

1 Team members

- Moataz Elbayaa " moataz.elbayaa@stud.hshl.de "
- Ahmed Helmy " ahmed.helmy@stud.hshl.de "
- Manoj Luitel " manoj.luitel@stud.hshl.de "
- Saikot Das Joy " saikot-das.joy@stud.hshl.de "

2 Introduction

Our Project is the extension of 4 bit Arithmetic Logic Unit(ALU) . Normally an ALU can do all the logic operations (Binary and, or, and, nor, xor, xnor, inverter etc) . But in our project, We have also included Binary Addition, Substraction, Multiplication and Division in 4 Bit ALU. We have used VHDL to design such a 4 bit ALU. We have used VHDL because it permits the behavior of the system to be verified and modeled in advance of the synthesis tools translation of the design into actual gates and wires (hardware).

FPGAs or Field Programmable Gate Arrays are semiconductor chips which are exactly as the name suggests – gate arrays that be configured in the field by the designer based on the needs. It consists of many configurable logic blocks which can be programmed based on what functions the designer requires it to perform.

3 Concept description

 


Fig: Block Diagram

Our designed Complex ALU, takes two 4 bit binary number as input and it also takes 4 bit SEL number as input. Based on the SEL number, it performs different operations. For example: it performs Binary "AND" operation for the SEL input "0000", "OR" operation for SEL input "0001", "NAND" operation for SEL input "0010", "NOR" operation for SEL

input"0011", "XOR" operation for SEL input"0100", "XNOR" operation for SEL input"0101", "NOT" operation for SEL input"0110". It also does Binary "ADDITION" operation for SEL input "1001", "Subtraction" operation for SEL input "1010", "MULTIPLICATION" operation for SEL input"0111" and "DIVISION" operation for SEL input "1000". All the output is found in 4 bit output "Y" except Multiplication. Multiplication output is found in output "MUL". The reminder of division is found in Output "Re" .

4 Project/ Team Management

At first, we made a list of tasks that needs to be done. Then individual team members shared their interests in which tasks they want to do. Then individual team members took the responsibility to perform specific tasks. How did we divide the task is found below:

Saikot Das Joy: VHDL code and VHDL test bench and RTL Schematic creation using Xilinx

Manoj Luitel : Schemetic design in Eagle

Moataz Elbayaa : Schematic design in Eagle and after that PCB design


Ahmed Helmy : PCB design

5 Technologies

We will use VHDL code to design our project. For this purpose, we will use A software name "Modelsim" . We will also use another software "XILINX ISE 14.7" to get the rtl schemetic. We will also use a software named "Eagle" to draw the schematic and PCB circuit board.

6 VHDL Implementation

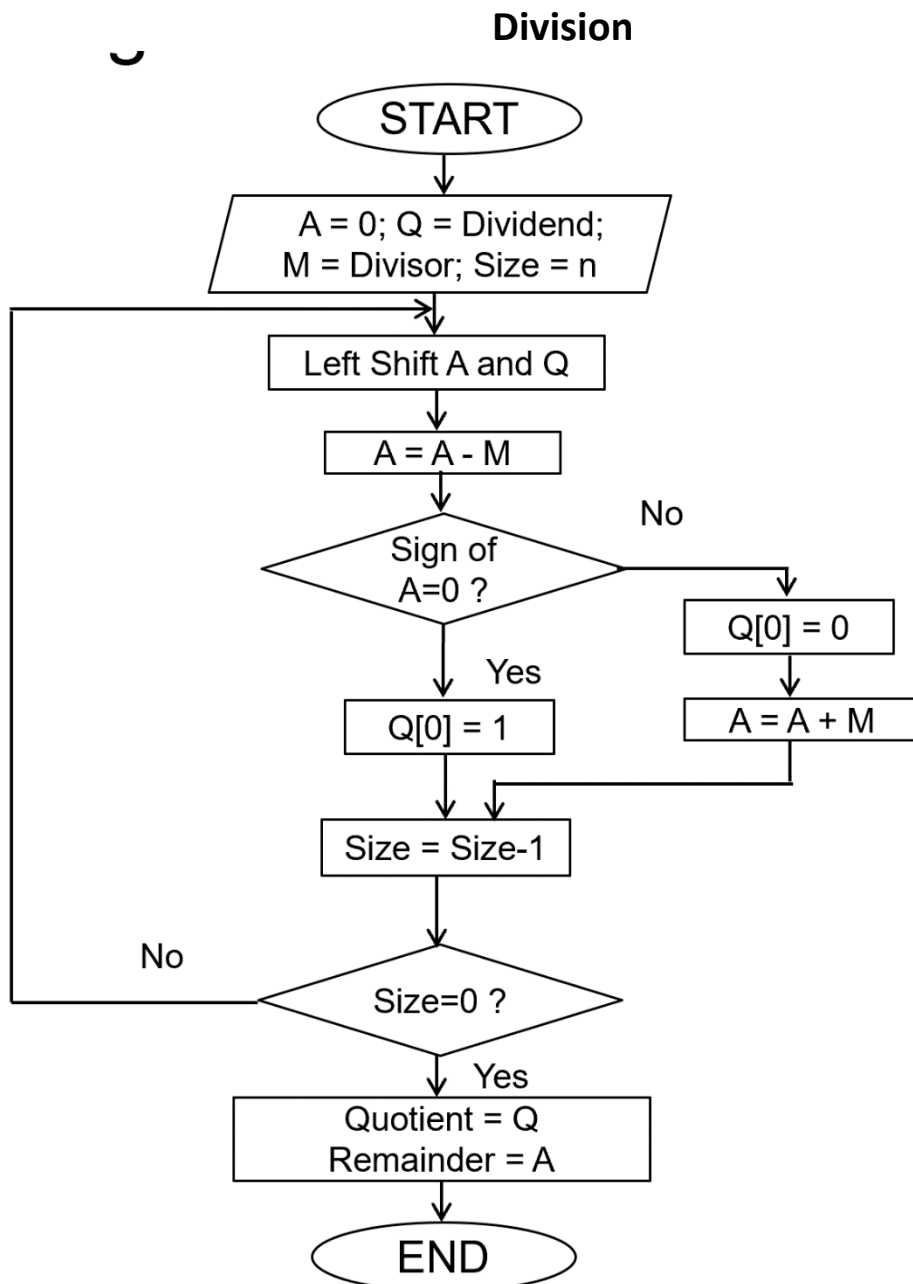
Here, in our project, The most complex part is 4-bit binary multiplication and division. So, This algorithm are described below:



Restoring Division Example

M = 3, Q = 7		M = 0011	
Q = 0111		-M = 1101	
A	Q	Size	Comment
0000	0111	4	initialize
0000	111□	4	Left Shift A and Q
1101			
1101	111□	4	A=A-M
0011			
0000	1110	3	Set Q[0]=0 and A=A+M
0001	110□	3	Left Shift A and Q
1101			
1110	110□	3	A=A-M
0011			
0001	1100	2	Set Q[0]=0 and A=A+M
0011	100□	2	Left Shift A and Q
1101			
0000	100□	2	A=A-M
0000	1001	1	Set Q[0]=1
0001	001□	1	Left Shift A and Q
1101			
1110	001□	1	A=A-M
0011			
0001	0010	0	Set Q[0]=0 and A=A+M
Remainder	Quotient		


Multiplication:

 

1 0 1 0	→	Multiplicand
× 1 0 1 1	→	Multiplier
1 0 1 0	→	Partial product 1
1 0 1 0	→	Partial product 2
0 0 0 0	→	Partial product 3
1 0 1 0	→	Partial product 4
1 1 0 1 1 1 0		

7 RTL Schematic

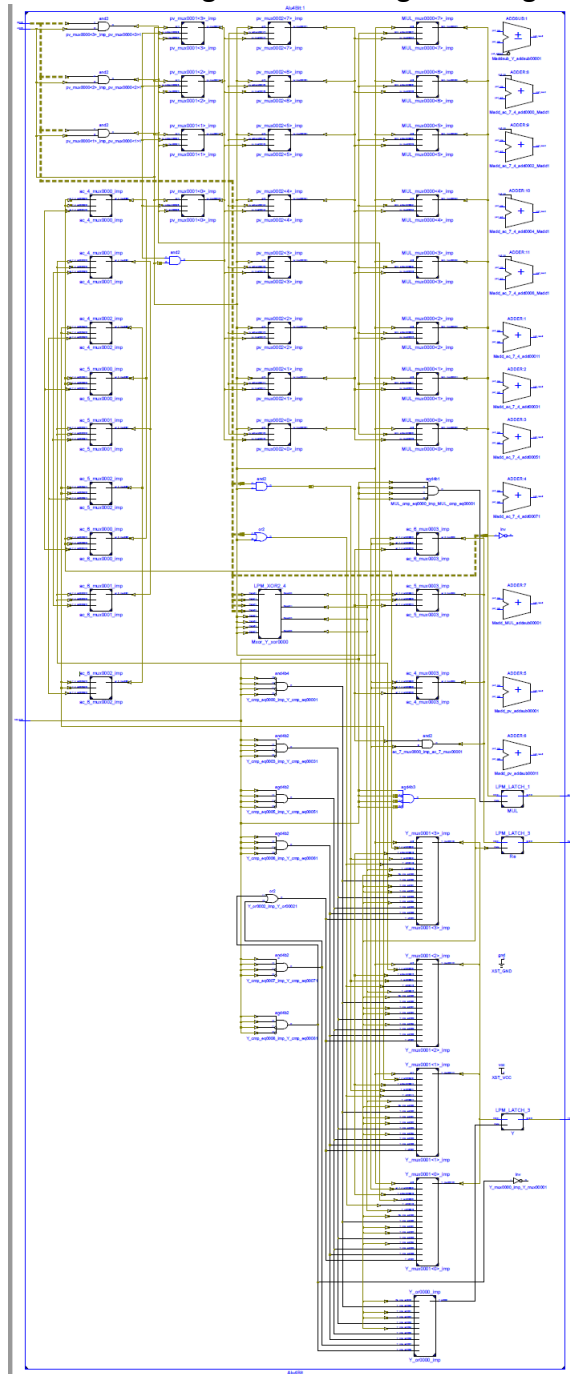RTL schematic generated using Xilinx is given below:



It is quite impossible to view this as an image file. You can find this diagram as a pdf file with High resolution Github.

8 Source Code

The VHDL code and test code is given below: (in Github Also)

VHDL: (Source Code)

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
use IEEE.STD_LOGIC_arith.ALL;

entity ALULULU is
    Port ( A      : in  STD_LOGIC_VECTOR (3 downto 0);  --- First Number Input
          B      : in  STD_LOGIC_VECTOR (3 downto 0);  ----- 2nd number input
          Y      : out STD_LOGIC_VECTOR (3 downto 0);  --- Output for all operation
    except multiplication
          MUL     : out STD_LOGIC_VECTOR (7 downto 0);  --- output for multiplication
          Re      : out STD_LOGIC_VECTOR (3 downto 0);  --- Reminder after division
    operation
          SEL     : in  STD_LOGIC_VECTOR (3 downto 0));  --- selection input to do
    specific operation
end ALULULU;

architecture Behavioral of ALULULU is

begin
    ALULULU_Proc : Process(A,B,SEL)
        variable ac : STD_LOGIC_VECTOR(7 downto 0);  --- variable declation for division
    operation
        variable Mbar : STD_LOGIC_VECTOR(3 downto 0);  ---- variable declation for Division
    operation
        variable pv,bp : STD_LOGIC_VECTOR(7 downto 0);  ---- variable declation for
    Multiplication operation
    Begin
    Case SEL is
    When "0000" =>
        Y <= A and B;
    When "0001" =>
        Y <= A or B;
    When "0010" =>
        Y <= A nand B;
    When "0011" =>
        Y <= A nor B;
    When "0100" =>
        Y <= A xor B;
    When "0101" =>
        Y <= A xnor B;
    When "0110" =>
        Y <= not A;
    
```

When "0111" => ----- Multiplication

```
        pv := "00000000";
        bp := "0000" & B;
    for i in 0 to 3 loop
        if a(i) = '1' then
            pv := pv + bp;
        end if;
        bp := bp(6 downto 0) & '0';
    end loop;
    MUL <= pv;
```

When "1000" => ----- Division

```
    Mbar := not B;
    ac := "0000" & A;
    for i in 1 to 4 loop
        ac(7 downto 0) := ac(6 downto 0) & '0';
        ac(7 downto 4) := ac(7 downto 4) + Mbar + "0001" ;
        if ac(7) = '1' then
            ac(0) := '0' ;
            ac( 7 downto 4) := ac(7 downto 4) + B;
        else
            ac(0) := '1';
        end if;
    end loop;
    Y <= ac(3 downto 0);
    Re <= ac(7 downto 4);
```

When "1001" => ----- Addition

```
    Y <= (A + B);
```

When "1010" => ----- Substraction

```
    Y <= (A - B);
when others =>
    NULL;
end case;
end process;
end Behavioral;
```

VHDL Test Bench :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;
use IEEE.STD_LOGIC_arith.ALL;
```

```
entity ALULULU_TB is
```

Hammer

end entity;

architecture CTB of ALULULU_TB is

component ALULULU

```
port (A : in std_logic_vector(3 downto 0);
      B : in std_logic_vector(3 downto 0);
      SEL : in std_logic_vector(3 downto 0);
      Y : out std_logic_vector(3 downto 0);
      MUL : out std_logic_vector(7 downto 0);
      Re : Out std_logic_vector(3 downto 0));
```

end component;

```
signal A_TB : std_logic_vector(3 downto 0);
signal B_TB: std_logic_vector(3 downto 0);
signal SEL_TB : std_logic_vector(3 downto 0);
signal Y_TB : std_logic_vector (3 downto 0);
signal MUL_TB : std_logic_vector (7 downto 0);
signal Re_TB : std_logic_vector (3 downto 0);
```

begin

```
DUT1: ALULULU port map (A => A_TB , B => B_TB , SEL => SEL_TB, Y => Y_TB,
                        MUL => MUL_TB, Re => Re_TB);
```

```
A_TB <= "0000", "0010" after 100ns, "0100" after 200ns, "0110" after 300ns, "0011" after
400ns, "0011" after 500ns, "0011" after 600ns, "0011" after 700ns, "1010" after 800ns,
"1010" after 900ns,"1010" after 1000ns, "1010" after 1100ns, "1010" after 1200ns;
```

```
B_TB<= "0000", "0001" after 100ns, "0010" after 200ns, "0011" after 300ns, "0100" after
400ns, "0101" after 500ns, "0110" after 600ns, "0111" after 700ns, "1000" after 800ns,
"1001" after 900ns,"1010" after 1000ns, "1011" after 1100ns, "0110" after 1200ns;
```

```
SEL_TB<= "0000", "0001" after 100ns, "1000" after 200ns, "0011" after 300ns, "0100" after
400ns, "0001" after 500ns, "0011" after 600ns, "0010" after 700ns, "0111" after 800ns,
"0010" after 900ns, "0011" after 1000ns, "0000" after 1100ns, "0001" after 1200ns;
```

end CTB;